

ADDING COLOUR TO THE ACE

Black and white is boring, so add a little colour (or a lot, if you want) to your computer's life with this project from John Wike. Additional material by Phil Walker.

The two facilities that really enhance the output of a microcomputer are sound and colour. The Jupiter Ace already has sound of sorts and this project provides a means of adding colour to its monochrome display. Eight colours including white and black are available, any of

which may be selected as foreground (ink) or background (paper). The circuit is active from switch-on and requires no special software for monochrome operation. Thus programs may be listed, edited and run without the need to keep swapping over aerial leads or operating systems. The board uses the smaller edge connector and contains a RAM (addressed in parallel with the Ace video RAM) to hold the colour information for each of the 768 locations on the screen.

paper. The attribute number is obtained by adding the ink value to the paper value and adding 128 (80h).

Colour	Ink	Paper
Black	0	0
Blue	1	16 (10h)
Red	2	32 (20h)
Purple	3	48 (30h)
Green	4	64 (40h)
Cyan	5	80 (50h)
Yellow	6	96 (60h)
White	7	112 (70h)

EDITORIAL COMMENT

It may seem a little strange to publish a project for the Jupiter Ace several months after the manufacturer has gone into liquidation. However, there will be a number of readers around who have Aces, and, moreover, we think that there is a lot to be learned from the techniques and systems described here. We think you will agree with us once you've read this article.

Attributes

Each character written on the screen will have associated with it the current attribute describing its ink and paper colours. To print anything with different colours the current attribute must first be updated. This is easy to implement and software for doing so is given later. The default colours at switch-on are green ink and black

About The Ace

The Jupiter Ace video display consists of 24 rows of 32 characters, each of which is selected by storing the required code at the appropriate location in the video RAM. There are 128 character shapes (plus their inverses) available and these are re-definable by the user.

At the rear of the computer

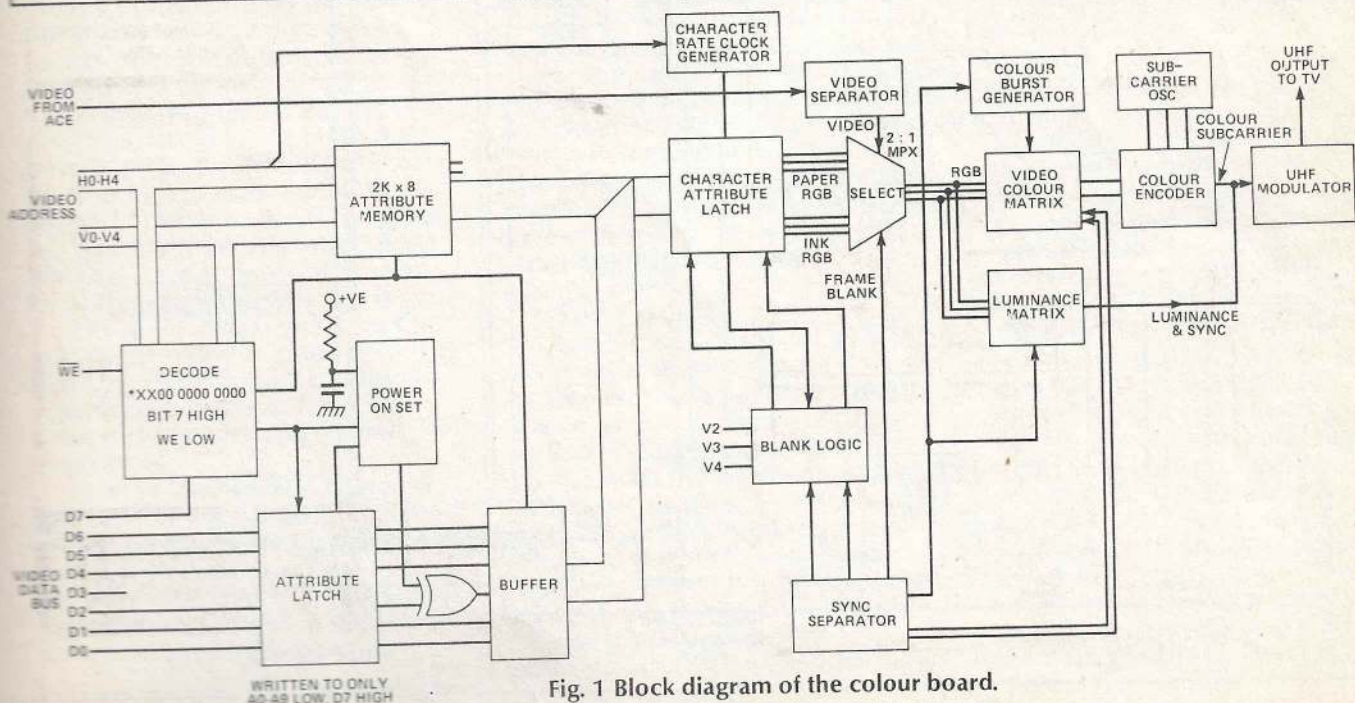


Fig. 1 Block diagram of the colour board.

Painting In Colours

To produce on a suitable TV set while still being able to get a good black and white picture from the same input signal, the broadcast authorities have adopted the PAL system for use in the UK. This system operates by retaining a simple amplitude modulated brightness (or luminance) signal which can be used by both colour and monochrome receivers. The colour information is added on to this in a rather complex manner such that it produces a minimum amount of interaction on the screen.

As far as our eyes are concerned, the colour information can be represented by the sum of three 'primary' colours — red, green and blue — in various mixtures. The total brightness effect of the combination is the luminance signal and this is transmitted as such.

The colour information is coded differently. The luminance signal is the weighted sum of all the colour signals and the colour information can be sent in two further difference signals obtained by subtracting the luminance signal from the red and the blue

colour signals. In order to combine these signals with the luminance signal, they are modulated onto sub-carrier signals. The frequency of the two sub-carriers is the same and has a carefully chosen relationship to the line frequency. The difference between the sub-carriers is that they are 90° out of phase with each other. This phase difference is $+90^\circ$ on one line and -90° on the next to reduce the visible effects of phase distortion during transmission. These modulated sub-carriers are then combined with the luminance signal to form the composite video signal. This, together with a separate frequency-modulated sound sub-carrier, is then used to modulate the UHF transmitter.

This, then, is what the colour board project is doing (with the exception of the sound part). Incidentally, there are a few other such as synchronising and blanking signals which have not been mentioned but are necessary and are provided by the circuitry on the PCB.

A Typical Video System

For those of our readers not yet thoroughly steeped in the inner

workings of micros from the hardware side, we present a short description of a typical black and white TV style video display.

As far as we can tell from a surreptitious peek inside the case of a Jupiter Ace borrowed for the occasion, there is nothing unusual about the video system used. Fig. 3 shows in block diagram form the main components of such a system.

The first major part to consider is the 1K of RAM which stores one 8-bit byte for each character location on the screen. This memory can be written into and read by the processor. By this means information can be updated as necessary.

The next part to consider is the video address generator. This normally consists of a crystal controlled clock oscillator driving a counter chain. The frequency of the oscillator and the division ratio of the counter chain are matched together such that they also provide information at the correct time for line and frame synchronising pulses and for the blanking signals necessary to prevent us seeing the line and frame fly-back traces.

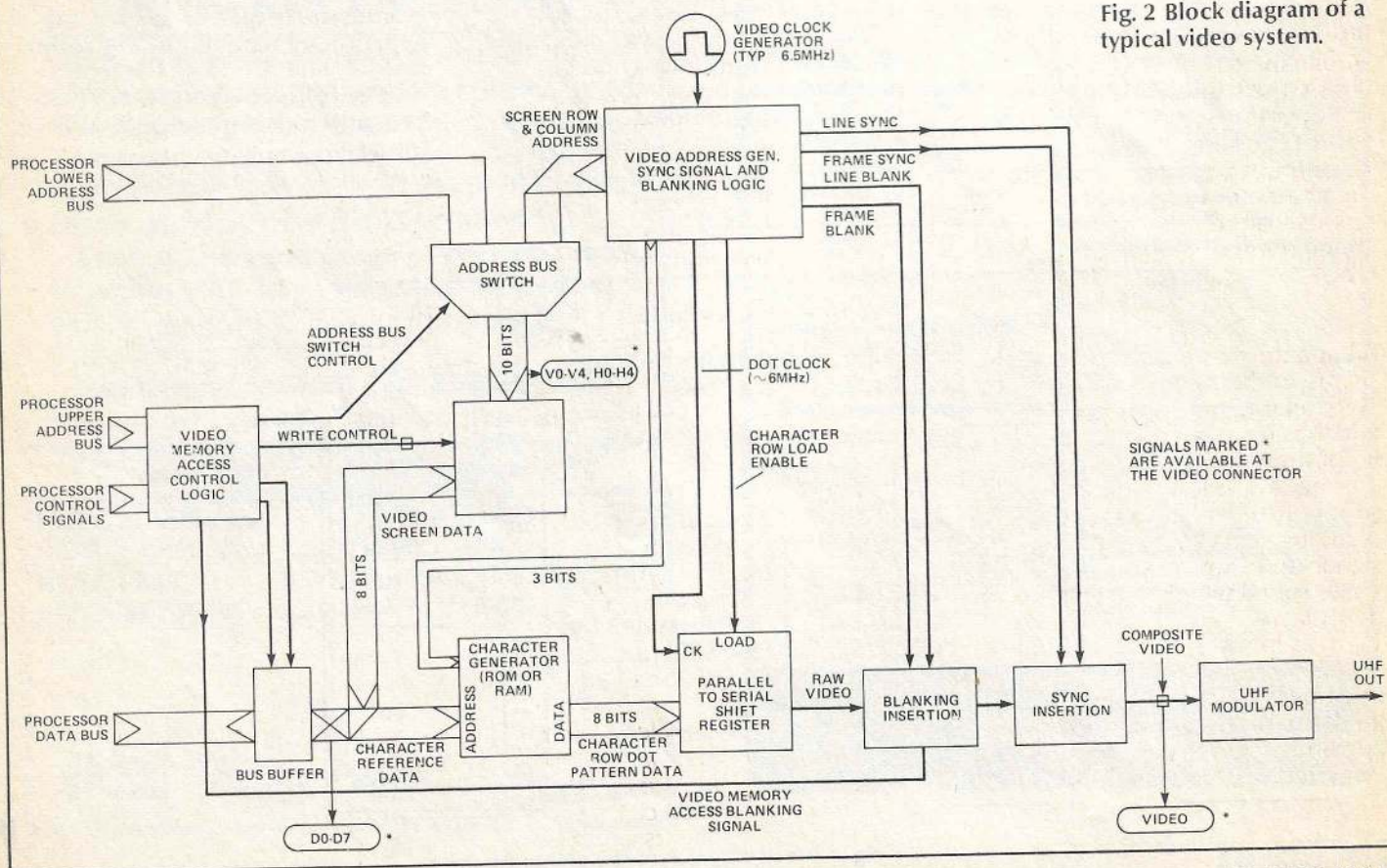


Fig. 2 Block diagram of a typical video system.

PROJECT : Adding Colour

For operation in the UK and several European countries, the line period is $64\mu\text{s}$ (15.625kHz) while the frame period is 20ms (50 Hz). The line blanking period is nominally $12\mu\text{s}$ while the frame blanking lasts about 4ms.

The video address generator in the Ace provides 5 address lines in the horizontal direction and 5 more for the vertical direction. This gives a possible 32×32 screen of which only 32×24 are actually used. In addition to these 10 address lines there are three more (sometimes four in other machines) which go directly to the character generator — of which more later.

When the video system is displaying the data in the video RAM at any time the address generator supplies 10 address bits to the RAM which then supplies its eight data bits on its output pins. These are taken to the character generator device. The character generator can be either ROM or RAM and in the case of the Ace it is RAM.

In the Ace, seven of the data bits from the video RAM are used as address bits for the character generator and point to a group of eight locations in it. These locations store the dot pattern for each horizontal line of the character specified by the seven bits from the video RAM. The actual line to be displayed is selected by the three extra address lines coming from the video address generator.

The dot pattern for the line of the character to be displayed passes from the output of the character generator to a parallel input shift register. At a suitable time the data is loaded into this device and then shifted out one bit at a time to give the raw video signal. In the Ace there is an extra bit available from the video RAM which is used to invert the polarity of the raw video when it is set.

The raw video signal from the shift register is combined with the blanking signals and then the sync. signals to form the composite video signal which drives the UHF modulator.

If, as in the Ace, the character generator is not a ROM, then there must be a way for the processor to load it with the correct dot patterns when the machine is first switched on. Note that this is not shown on the block diagram.

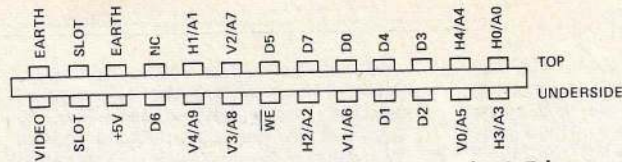


Fig. 3 Edge connector details that aren't in the manual!

there are two edge connectors, the larger of which is documented in the manual and brings out the processor busses for memory and peripheral expansion. The smaller connector is not documented, but it is intended for expansion of the video circuits and carries the video RAM address, data and WE lines as well as the composite video signal from the input to the UHF modulator.

The 1K video RAM appears twice in the Ace memory map, at 2000h-23FFh and at 2400h-27FFh. When addressed in the lower range the processor has priority over the video circuits and accesses can occur during the display period. In the higher range the video circuits have priority and processor accesses are confined to the blanking periods. The latter is the preferred situation so only the range 2400h-27FFh will be considered here.

Of this space the 768 bytes at 2400h-26FFh hold the screen data and the 255 bytes at 2701h-27FFh are used as a scratchpad by the system. According to the ACE manual, the one remaining byte at 2700h should always be zero, but this is in fact used only by the input command interpreter to mark the end of the input buffer on the screen. Therefore when a program is running, the byte can be any value provided it returns to zero before the next operation of the command interpreter. Thus the current colour attribute is held in a latch at 2700h. As a zero written to this address must not affect the contents of the latch, the most significant data bit D7 is set to 1 (by adding 128) to indicate that an attribute is to be stored.

The Circuit

The circuit consists of a six-bit current attribute latch, a 1K by 6 screen attributable RAM, a blanking section, ink/paper selector, colour encoder and UHF modulator. Both the latch and RAM are write only so it will be necessary to maintain separate variables or arrays to keep a check on their contents. In most situations, however, the value required in a particular RAM location can be derived from either its address or

the contents of the video RAM at that location.

As there is no blanking signal from the edge connector, it must be re-constituted from the RAM address counters. This can be done provided processor accesses are confined to the blanking periods by using addresses 2400h-27FFh as described earlier.

The selection of ink or paper is determined by the Ace video signal. Areas of the display that are normally white are taken to be ink and black areas to be paper.

The colour encoder is based on a National Semiconductor LM1889 colour modulator chip. Although designed to work at the American colour subcarrier frequency of 3.58MHz, it will work at the UK's 4.4336MHz with suitable changes of component values. This IC requires a supply voltage of 10 to 15 volts, for which the author used a spare computer power pack which actually came with a Sinclair printer. Obviously any alternative voltage source could be used. The 5 volt supply for the UHF modulator was derived from the 12 volt line to avoid problems with noise on the logic supply.

Construction

Construction of this project is straightforward but we recommend that you do it in the following order using a fine tipped soldering iron.

Firstly, since this is a double sided PCB and is not plated through, some links must be inserted and soldered on **both** sides of the board; note especially the ten underneath IC8. Also, some component leads must be soldered on both sides.

Next fit the recommended IC sockets for IC8 and IC14. Now fit the other ICs and remember to solder the leads on the top, bottom or both sides of the board as necessary. Check this part carefully as mistakes here will be very difficult to locate. Make very sure you put ICs in the right way round as well.

Now fit the resistors, capacitors, variable resistors, variable capacitor, diodes, transistors, crystal, edge connector and UHF modulator in this order. Don't forget

The address inputs of RAM IC8, the colour attribute store, are connected to the address inputs of the Ace video RAM, H0 to H4 and V0 to V4. These lines normally carry the display horizontal and vertical character position counters, but during a processor access to the video RAM (2400h — 27Fh) they are equal to the processor address lines A0 to A9.

If the access is a write operation then the decoded write enable signal WE will go low and data from latch IC4 (via tri-state buffer IC1) will be written into IC8. The WE signal is further decoded by gates IC2 and IC3 so that data written to address 2700h will be latched in IC4 if the most significant bit D7 is high. At switch on, IC4 is cleared by R3/C5, but as this would give a colour attribute of black on black, gate IC6a (controlled by latch IC5b) inverts the green ink signal to give the default condition of green on black. Latch IC5b will be cleared when IC4 is written to, and the green ink signal will then be passed normally by IC6a.

During the display period, gates IC6b

and c in conjunction with output Q2 of latch IC11 produce a short clock pulse for IC11 every time address line H0 changes. As the RAM outputs change very quickly, timings here are critical so H0 is buffered by IC1b and H1 is delayed slightly by C2.


The outputs of IC11 consist of three ink bits and three paper bits for the character currently being displayed by the Ace character generator. Selection of ink or paper bits in data selector IC12 is controlled by Schmidt trigger Q2/3 from the Ace composite video signal. White areas select ink colours and black areas select paper colours. The outputs of IC12 are the red, green and blue video signals.

The most significant horizontal address line H4 clocks bistable IC10a on and off to provide line blanking. To ensure that any processor accesses of the video RAM during the blanking period do not lead to incorrect trigger-



ing of IC10a, monostable IC7 and differentiator R11/C9 give a short window for triggering to occur. Latch IC5d and output Q1 of IC11 serve to delay the blanking signal for the same period that the data from the RAM is delayed.

Sync separator Q1/IC1d provides the line sync for the board from the Ace composite video signal. The sync is integrated by R12/C11 to give a field sync input to set latch IC5c, the field blanking generator. The latch is reset by a short pulse produced by differentiator C9/R9/R10 at the end of one cycle of address line V2. This allows the field display period, which ends when address lines V3 and V4 (combined in IC5a wired as a NAND gate) are both high and sets IC5c again. Integrating networks R13/C10 and R2/C4 prevent their respective signals responding to changes caused by processor accesses, as these last only about 1µs.

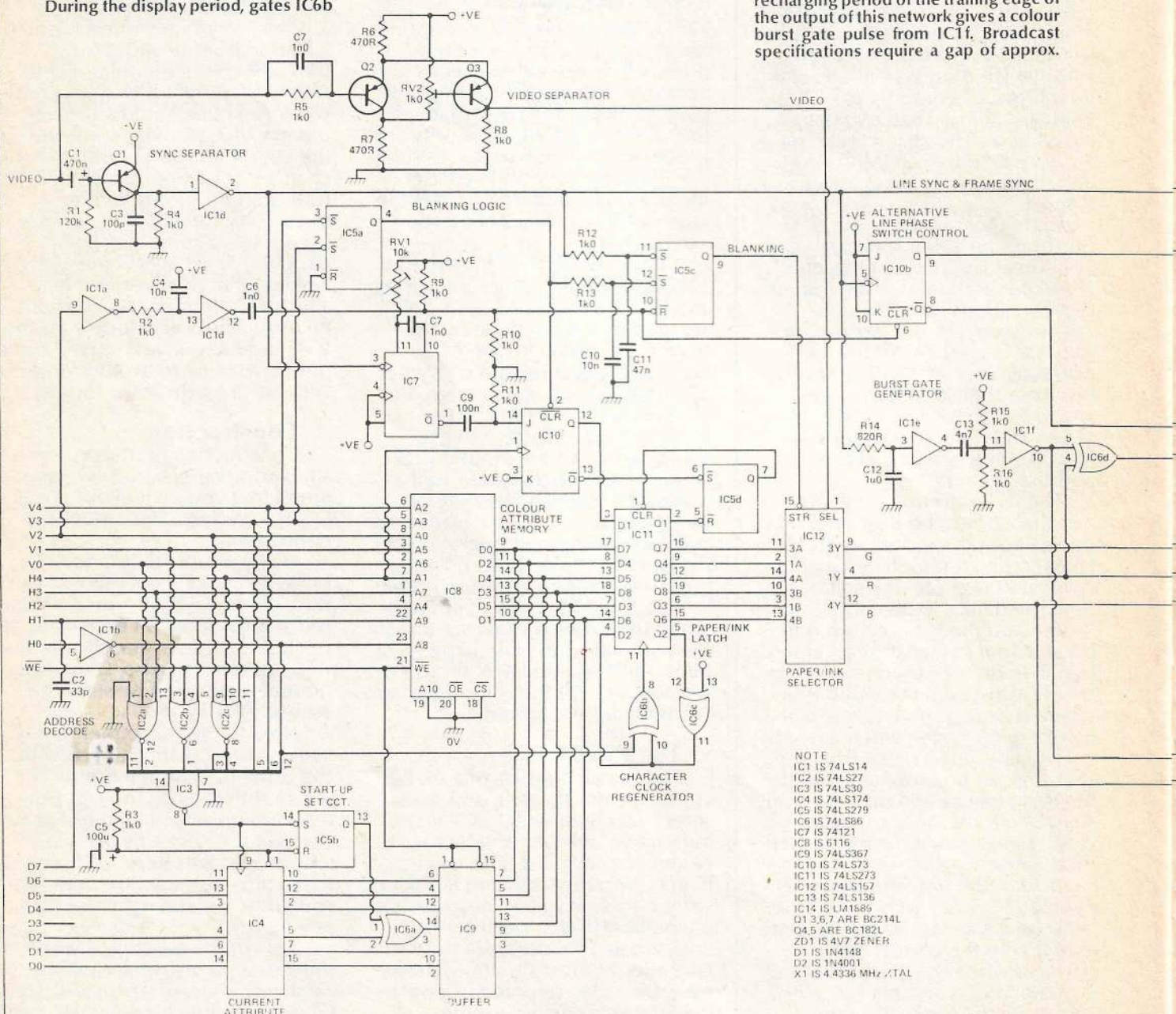The line sync pulse is applied via R1d to differentiator C13/R15/R16. The recharging period of the trailing edge of the output of this network gives a colour burst gate pulse from IC1f. Broadcast specifications require a gap of approx.



WORKS

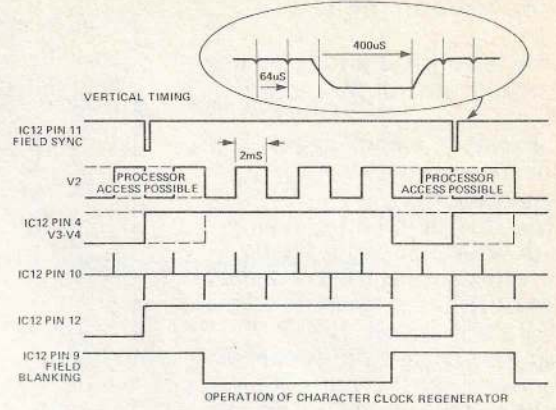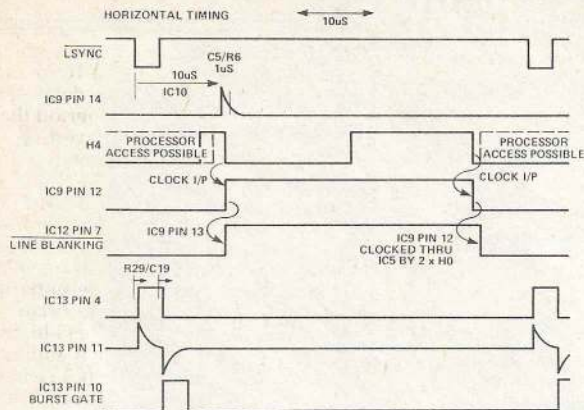

800ns between line sync and burst. This is provided by delay network R14/C12.




Bistable IC10b is clocked by the line sync to give the PAL alternating phase control. This was found to require phase locking to the field period in order to work with the author's TV so the short differentiated V2 signal at C6/R15/R10 was available to clear the bistable.

The red, green, blue and sync signals are combined in R21,30,31,36,37,38, 39 and D1 to give the composite grey-scale luminance signal. This is applied

via output stage Q6 and Q7 to the UHF modulator. A relatively clean 5 volt supply for the output stages is derived from the 12 volt supply by R41/ZD1.

The colour subcarrier is generated by colour modulator IC13 at a frequency determined by the feedback network around pins 18 and 17, set by crystal X1 at 4.433 MHz. The phase shifting networks R33/C17 and C16/R17 ensure that the inputs at pins 1 and 18 have a phase difference of 90° to form the quadrature components of the subcarrier. These are modulated respectively by the R-Y and B-Y colour difference signals at pins 2 and 4. For the limited range of colours to be displayed, the difference signals can be produced by algebraically subtracting the red and green and the blue and green colour signals. This is achieved by the open collector gates of IC13 switching current into the emitters of Q4 and Q5. The values of bias resistors R27/R28 and R25/R26 ensure that the zero level of the difference signals is equal to the chrome bias voltage at IC14 pin 3.

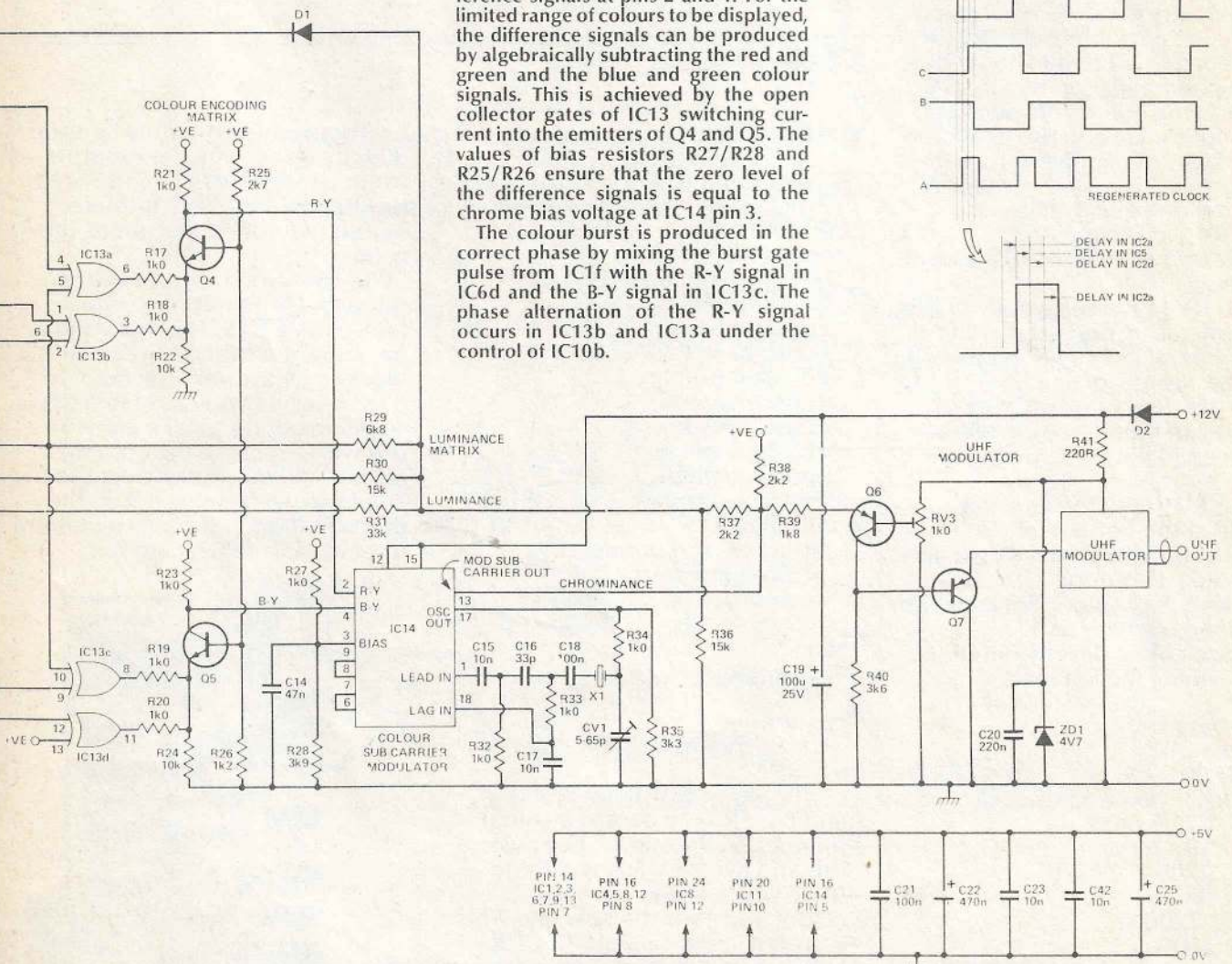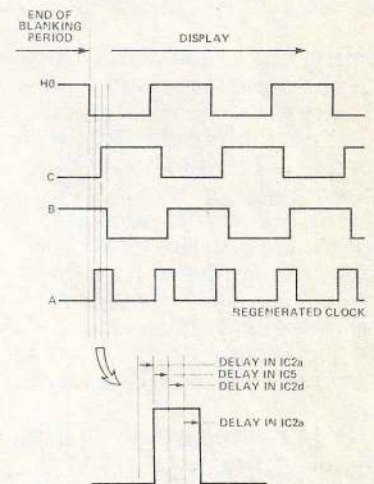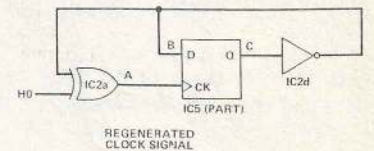The colour burst is produced in the correct phase by mixing the burst gate pulse from IC1f with the R-Y signal in IC6d and the B-Y signal in IC13c. The phase alteration of the R-Y signal occurs in IC13b and IC13a under the control of IC10b.



the flying leads for the 12 volt supply.

Lastly, insert IC8 and IC14 in their sockets and all should be ready.

At this stage, **check again** carefully for shorted tracks, etc, before setting up.

If you do not get a polarising key with your piece of edge connector, either bend the contacts at the slot position in towards each other or alternatively, break the pins off very close to the rear of the connector at the correct position and pull the contact part out of the front.

Cut a small piece of PCB material or similar board and having made sure that it fits the slot in the Ace connector, glue it, preferably with a fast-acting cyanoacrylate adhesive, into the front of the edge connector. This will allow positive location of the connector into the Ace.

Setting Up

After checking the board (again!) very carefully for shorted tracks, etc plug it into the Ace, connect it to a 12 volt supply (that is switched off!), connect the TV aerial to the board and switch on all supplies. Tune in the television and a blank flickering raster should be present.

Now proceed as follows:

Turn RV2 fully clockwise.

Adjust RV3 so that the blank raster is locked.

Adjust RV1 until the whole display area brights up and set it at the mid point of its bright-up range. It may be necessary to adjust RV3 to keep the display steady. The central area of the screen should now be green. If not try re-tuning the TV.

Adjust RV2 until the cursor is visible at the bottom left.

Enter VLIST and adjust RV2 to give the boldest lettering with no streaking. Any colour dot crawl can be tuned out with CV1.

Produce colour bars by entering and running the following:

```
16 base c!
: colourbars
2700 2400
do
i 4 / 8 mod
10 * 80 or
2700 c! 20 i c!
loop
87 2700 c!
0 2700 c!
```

Adjust RV3 to give the best range of colours.

PARTS LIST

RESISTORS (all 1/4W 5% unless stated)

R1	120k
R2-5, 8-13, 15-21	
23, 27, 32-34	1k0 (22 off)
R6, 7	470
R14	820
R22, 24	10k
R25	2k7
R26	1k2
R28	3k9
R29	6k8
R30, 36	15k
R31	33k
R35	3k3
R37, 38	2k2
R39	1k8
R40	3k6
R41	220, 1/2W
RV1	10k 10-turn preset
RV2, 3	1k0 preset
CAPACITORS	
C1, 22, 25	470n 35V tant
C2, 16, 17	33p
C3	100p
C4, 10, 15, 23, 24	10n
C5	100µ 6V3 electrolytic
C6, 7, 12, 9	1n0
C 11, 14	47n
C 18, 21	100n
C13, 8	4n7
C19	100µ 25V electrolytic

C20	220n
CV1	5-65p
SEMICONDUCTORS	
IC1	74LS14
IC2	74LS27
IC3	74LS30
IC4	74LS174
IC5	74LS279
IC6	74LS86
IC7	74121
IC8	6116
IC9	74LS367
IC10	74LS73
IC11	74LS273
IC12	74LS157
IC13	74LS136
IC14	LM1889
Q1-3, 6, 7	BC214L
Q4, 5	BC182L
ZD1	4V7 zener, 500 mW
D1	1N4148
D2	1N4001

MISCELLANEOUS

X1	4.4336 MHz crystal
UM1233 UHF modulator; 13-way 0.1" double-sided edge connector; 24-pin DIL socket; 18-pin DIL socket; PCB; pins for link-throughs (if preferred); wire, etc	

Software

In order to use the colour facilities within FORTH programs, it is necessary to define the following words:


```
decimal 16 base c!
2700 constant attriblatch
0 constant black
1 constant blue
2 constant red
3 constant purple
4 constant green
5 constant cyan
6 constant yellow
7 constant white
87 variable attrib
: combine
attrib c@ and or dup
attrib c! attriblatch c!
0 attriblatch c!
```

```
;
: ink
£0 combine
;
: paper
10 * 87 combine
;
```


By way of explanation, INK and PAPER both expect a colour number on the stack. They pass this and a mask value to COMBINE which masks out the old colour and adds the new one. This is stored in the variable ATTRIB and also in the latch. Zero is then written to the latch for the reasons given earlier.

These words can now be used directly by entering for example white paper blue ink, or they can be liberally sprinkled at the required points in applications programs.

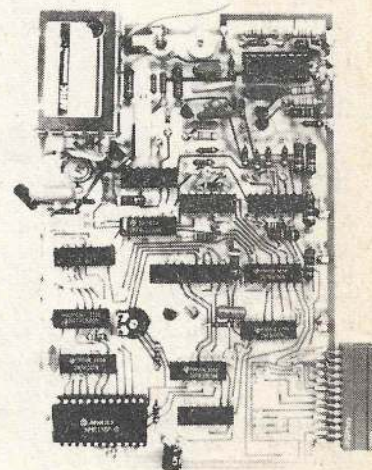If when you first turn on the screen is full of random colour blocks, do a CLS. This will write the current attribute (green on black) over the whole screen. Beware when you cause or allow a scroll operation to take place as this will also cause the current attribute to be written over the whole screen, wiping out all the pretty colours and giving a uniform foreground and background.




PROJECT : Adding Colour

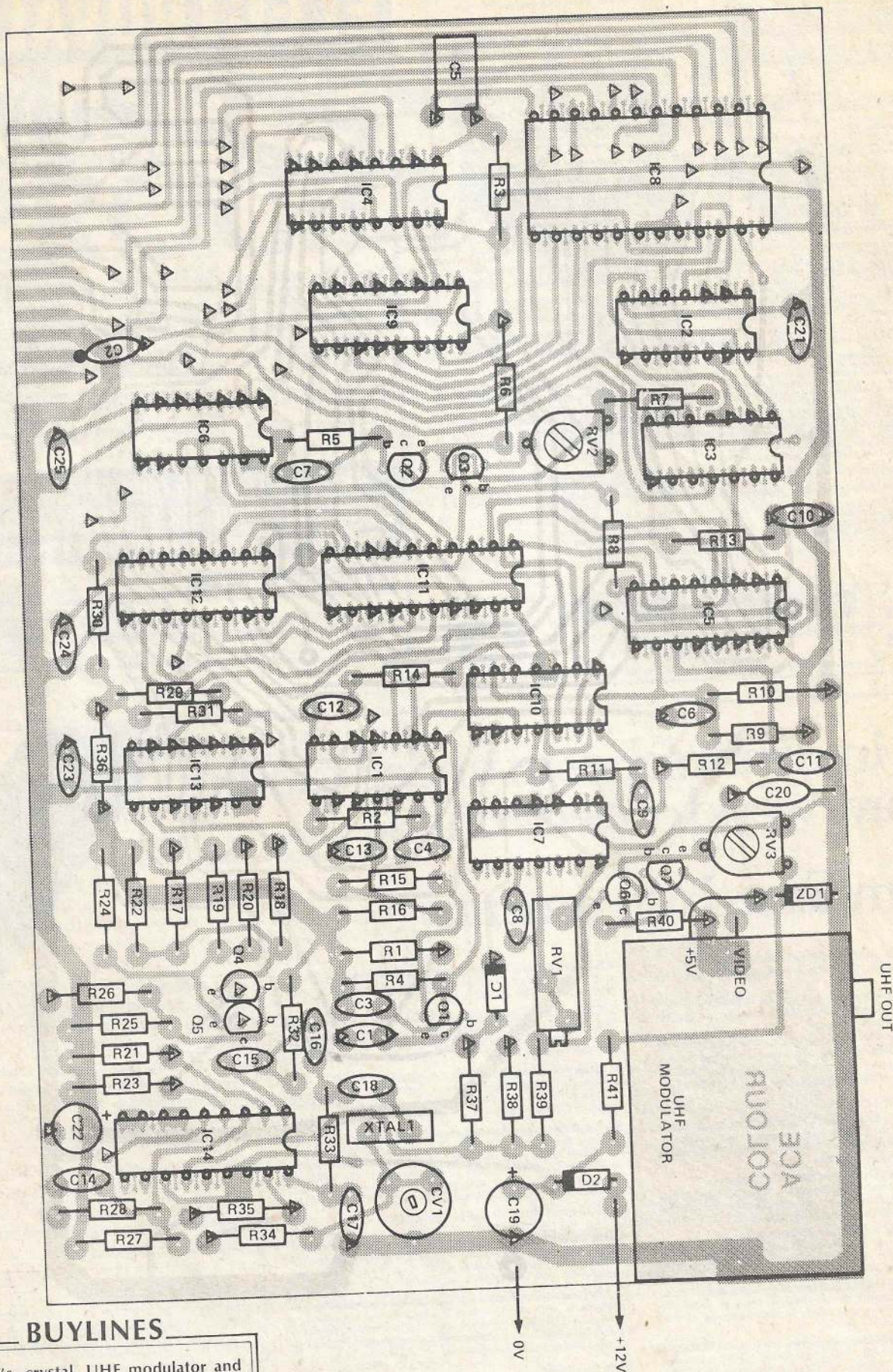

BUYLINES

The IC's, crystal, UHF modulator and the edge connector are all available from advertisers in ETI. The PCB is available from the author at 9 Lon y Garwa, Caerphilly, Mid-Glamorgan for £12 including postage.

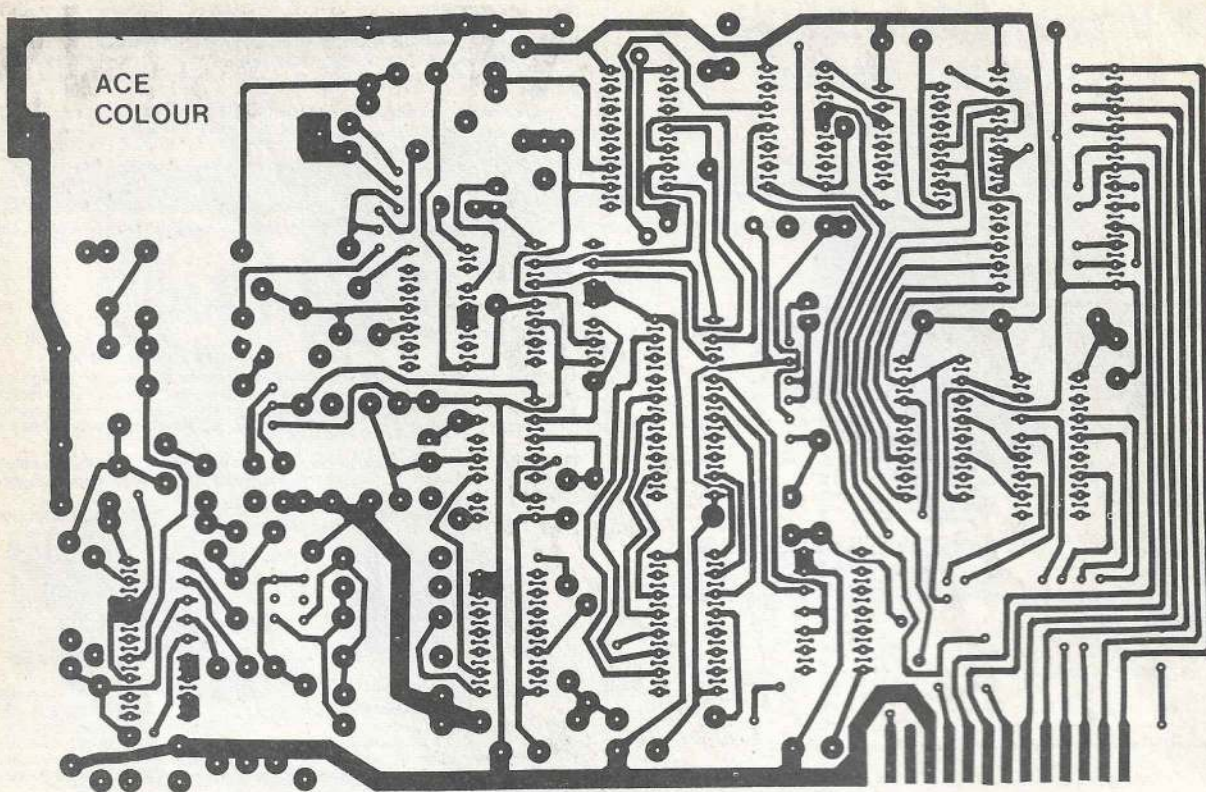- △ = SOLDERED ON BOTH SIDES (COMPONENTS AND LINKS)
- = SOLDERED TO TOP FOIL ONLY, WITH NO LEAD THROUGH



The Ace Colour Board.

